

tutorial 2

Dhananjay Joshi

example 1

A $100 \mu\text{A}$ meter movement with an internal resistance of 800Ω is used in $0-100 \text{ mA}$ ammeter.

Find the value of the required shunt resistance.

Here,

$$R_{sh} = \frac{I_m \cdot R_m}{I_{sh}}$$

$$R_{sh} = \frac{100 \times 10^{-6} \times 800}{100 \times 10^{-3} - 100 \times 10^{-6}}$$

$$R_{sh} = \frac{8 \times 10^4 \times 10^{-6}}{100 \times 10^{-3} [1 - 1 \times 10^{-3}]}$$

$$R_{sh} = \frac{8 \times 10^{-2}}{100 \times 10^{-3} \times 0.999}$$

$$R_{sh} = \frac{8 \times 10^{-2}}{0.99}$$

$$R_{sh} = \frac{8.080 \times 10^{-2}}{0.808 \text{ m}\Omega}$$

example 2

A PMMC instrument gives full scale deflection reading 25 mA when a potential difference across its terminal is 75 mV . show how it can be used (a) as an ammeter for the range of $0-100 \text{ A}$ (b) as a voltmeter for the range of $0-750 \text{ V}$. Also find the multiplying factor of shunt & voltage amplification.

Instrument resistance $R_m =$

Potential drop across terminals
instrumental current

$$= \frac{75 \times 10^{-3}}{25 \times 10^{-3}} = 3 \, \Omega$$

a] current to be measured $I = 100 \text{ mA}$

Multiplying power of shunt $I_m =$



$$= \frac{100}{25 \times 10^{-3}} = \underline{\underline{4000}}$$

shunt resistance required for full scale deflection, 100 A:

$$R_{sh} = \frac{R_m}{m-1} = \frac{3}{3999}$$

$$= 7.5 \times 10^{-4}$$

$$R_{sh} = 0.75 \text{ m}\Omega$$

b] Voltage to be measured $V = 750 \text{ V}$

$$R_{se} = \frac{V}{I_m} - R_m = \frac{750}{20 \times 10^{-3}} - 3 = 29.997$$

$$\text{Voltage application} = \frac{750}{75 \times 10^{-3}} = 10000$$

Q3. A moving coil instrument gives a FSD. of 10 mA & Potential difference across its terminal is 200 mV.

cal. (a) shunt resistance for FSD corresponding to 200 A (b) series resistance for full reading consumption to 2000 V.

Ans:-

Instrument resistance R_m .

Potential drop across terminal instrument current.

$$= \frac{100 \times 10^{-3}}{10 \times 10^{-3}} = 10 \Omega$$

a) shunt resistance required for FSD corresponding is 200 A.

$$R_{sh} = \frac{R_m}{\frac{I}{I_m} - 1} = \frac{10/200}{\frac{200}{100 \times 10^{-3}} - 1}$$

$$= 5.00025 \times 10^{-4} \Omega$$

A series resistance required for fSD corresponding to 1000V.

$$R_{se} = \frac{V}{I_m} - R_m = \frac{1000}{10 \times 10^{-3}} - 10$$

$$= 99.990 \Omega$$

Q.4

A Moving coil instrument having internal 50Ω indicate fSD with a (current of 10 mA). How can it be made to work as 1) a voltmeter to read 100 V on full scale deflection 2) on ammeter of 1 A on full scale.

internal resistance = 50Ω
current flowing through the instrument fSD $I_m = 10 \text{ mA} = 0.01 \text{ A}$

series resistance required to measure $R_{se} = \frac{V}{I_m} - R_m$

$$= \frac{100}{0.01} - 50$$

$$= 9950 \Omega$$

(ii) shunt required to measure 1 A current

$$R_{sh} = \frac{R_m}{\frac{1}{I_m} - 1} = \frac{50}{\frac{1}{0.01} - 1} = 0.5050 \text{ A } \Omega$$

Q.5

A moving coil instrument has a resistance of 2Ω & it reads upto 250 V when a resistance of 5000Ω is connected in series with it. find the current through other instrument when it is used as ammeter with the coil connected across a shunt resistance of $2 \text{ milli } \Omega$.

Ans:-

Resistance of the instrument coil
 $2\ \Omega$ current flowing through the
 instrument for
 FSD

$$I_m = \frac{\text{full scale reading}}{R + \text{series resistance}}$$

$$= \frac{250}{2 + 25000}$$

$$= 0.04998\text{ A}$$

shunt resistance $R_{sh} = 2 \times 10^{-3}\ \Omega$

current through shunt resistance

$$I_{sh} = \frac{I_m R_m}{R_s} = \frac{49.98 \times 10^{-3}}{2 \times 10^{-3}}$$

$$= \underline{\underline{49.98}}$$

current range of instrument:
 full scale.

Ans:-

Resistance of the instrument coil
 2Ω current flowing through the
 instrument for
 FSD

$$I_m = \frac{\text{full scale reading}}{R + \text{series resistance}}$$

$$= \frac{250}{2 + 25000}$$

$$= 0.04998 \text{ A}$$

shunt resistance $R_{sh} = 2 \times 10^{-3} \Omega$

current through shunt resistance

$$I_{sh} = \frac{I_m R_m}{R_s} = \frac{49.98 \times 10^{-3}}{2 \times 10^{-3}}$$

$$= \underline{\underline{49.98}}$$


current range of instrument =
 full scale.

Deflection
current.

$$= I_m + I$$

$$= 0.04998 + 49.98$$

$$= 50 \text{ A}$$

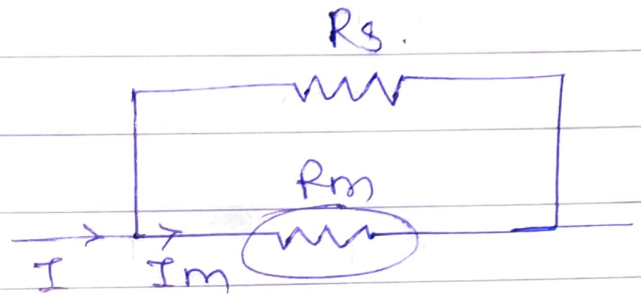

- Q.6 A moving coil ammeter gives f.s.d with 15 mA & has a resistance of 5Ω calculate the resistance to be calculated in as parallel to enable the instrument to read up to 1 A b) series to enable it to read up to 10 V.

instrument resistance $R_m =$

5Ω

$$\text{f.s.d} = \text{current } I_m = 15 \text{ mA} = 15 \times 10^{-3} \text{ A}$$

current to be measured 1 A.

shunt resistance to be connected in parallel.

$$R_{sh} = \frac{R_m}{\frac{1}{I_m} - 1} = \frac{5}{\frac{1}{15 \times 10^{-3}} - 1} = 0.07614 \Omega$$

voltage to be measured $V = 10V$

series resistance required

$$R_{se} = \frac{V}{I_m} - R_m$$

$$= \frac{10}{15 \times 10^{-3}} - 5$$

$$= 661.667 \Omega$$